
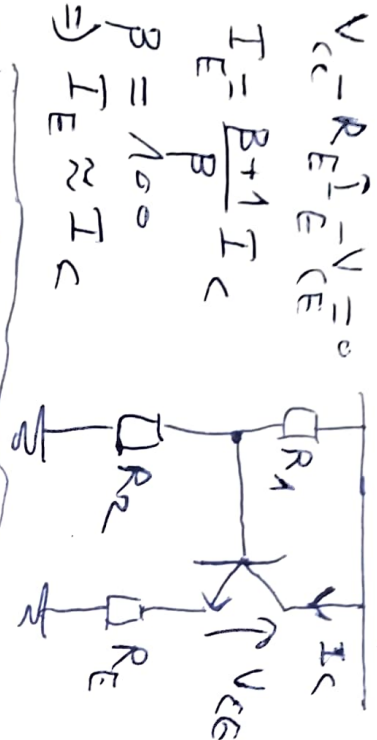


Exo 1 :


1) Droite de charge statique :

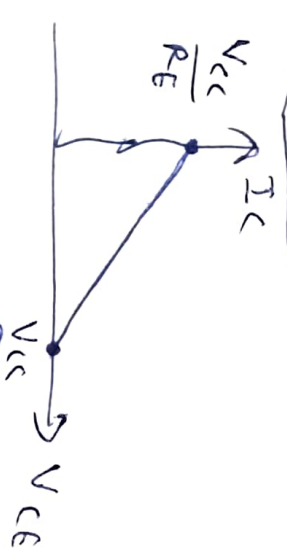

$V_{CE} - R_E I_E - V_{CE} = 0$
 $I_E = \frac{B+1}{B} I_C$
 $\Rightarrow I_E \approx I_C$
 $\Rightarrow I_C = -\frac{1}{R_E} V_{CE} + \frac{V_{CC}}{R_E}$



2) Coordonnées du point de repos :

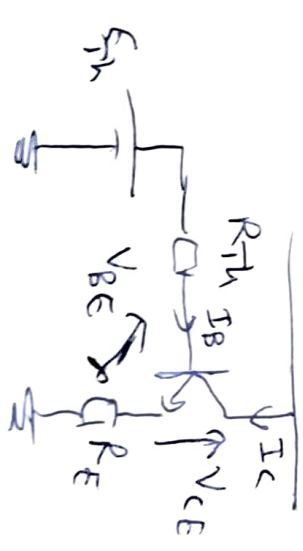

$R_{TH} = R_1 || R_2$
 $V_{BE} = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$

1


$E_{TH} = R_{TH} I_B - V_{BE} - R_E I_E = 0, V_{BE} \approx V_{BE0}, I_{CE} \approx I_C$
 $\Rightarrow I_B = \frac{E_{TH} - V_{BE0}}{R_{TH} + \beta R_E} \Rightarrow I_C = \beta I_B$

$\Rightarrow I_C = I_{CQ} = \beta \frac{E_{TH} - V_{BE0}}{R_{TH} + \beta R_E}$

$A.N. : I_{CQ} = 5.3 \text{ mA}$
 $V_{CE} = V_{CEQ} = V_{CC} - R_E I_{CQ} \approx V_{CC} - R_C I_{CQ}$

$A.N. : V_{CEQ} = 2.5 \text{ V}$

3) Résistances d'entrée :

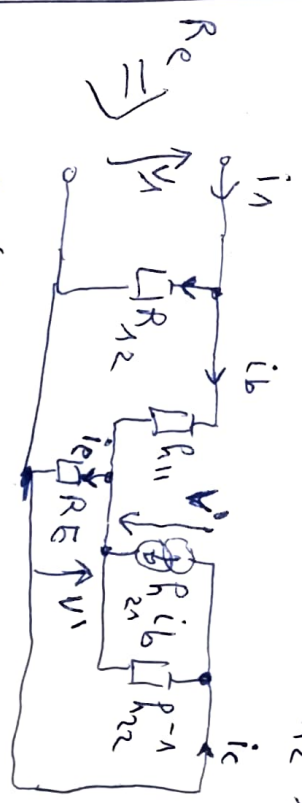

$V_1 = R_{12} (i_1 - i_b)$ — (1)
 $V_1 = R_{11} i_b + R_E i_e$ — (2)
 $V_1 = R_{22} i_e$ — (3)
 $V_1 = -R_{22} (i_c - R_{21} i_b)$ — (4)
 $i_e = i_c + i_b$ — (5)

2

$$(3) = (4) \Rightarrow R_E i_e = -R_{22}^{-1} (i_c - R_{21} i_b)$$

$$(5) \rightarrow (6): R_E (i_c + i_b) = -R_{22}^{-1} (i_c - R_{21} i_b) \quad (6)$$

$$\Rightarrow (R_E + R_{22}^{-1}) i_c = (R_{22}^{-1} R_{21} - R_E) i_b$$

$$\Rightarrow i_c = \frac{R_{21} R_{22}^{-1} - R_E}{R_E + R_{22}^{-1}} i_b \quad (7)$$

$$(9) \rightarrow (5) \quad i_e = \left(\frac{R_{21} R_{22}^{-1} - R_E}{R_E + R_{22}^{-1}} + 1 \right) i_b$$

$$\Rightarrow i_e = \frac{R_{21} R_{22}^{-1} + R_{22}^{-1}}{R_E + R_{22}^{-1}} \cdot i_b \quad (8)$$

$$(8) \rightarrow (8): V_1 = R_{11} i_b + R_E \cdot \frac{(R_{21} + 1) R_{22}^{-1}}{R_E + R_{22}^{-1}} i_b$$

$$\Rightarrow i_b = \frac{V_1}{R_{11} + R_E \cdot \frac{(R_{21} + 1) R_{22}^{-1}}{R_E + R_{22}^{-1}}} \quad (9)$$

3

$$(9) \rightarrow (1) =$$

$$V_1 = R_{12} i_1 - R_{12} i_2 \cdot \frac{V_1}{R_{11} + R_E \frac{(R_{21} + 1) R_{22}^{-1}}{R_E + R_{22}^{-1}}}$$

$$\Rightarrow V_1 \left[1 + R_{12} \cdot \frac{1}{R_{11} + R_E \frac{(R_{21} + 1) R_{22}^{-1}}{R_E + R_{22}^{-1}}} \right] = R_{12} i_1$$

$$\Rightarrow R_E i_1 = \frac{V_1}{R_{12}} \cdot \frac{1 + R_{12} \frac{1}{R_{11} + R_E \frac{(R_{21} + 1) R_{22}^{-1}}{R_E + R_{22}^{-1}}}}{1}$$

$$R_{22}^{-1} = \frac{V_A}{I_Q} = \frac{90}{5.13 \times 10^{-3}} \Rightarrow R_{22}^{-1} \approx 17.7 \text{ k}\Omega$$

$$R_{11} = \beta \frac{V_T}{I_Q} = 156 \cdot \frac{26 \cdot 10^{-3}}{5.13 \times 10^{-3}} = 768 \text{ }\Omega$$

$$\Rightarrow R_E \approx 13,48 \text{ k}\Omega \quad \text{à width}$$



4

~~3~~ R_e (en charge) = R_e (à vide)

$R_E \rightarrow R_E \parallel R_L$

R_e (en charge) = 11,45 k Ω

4) Résistance de sortie =

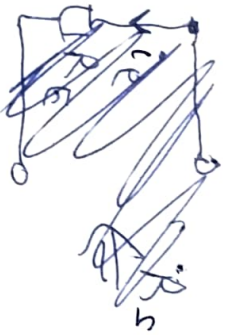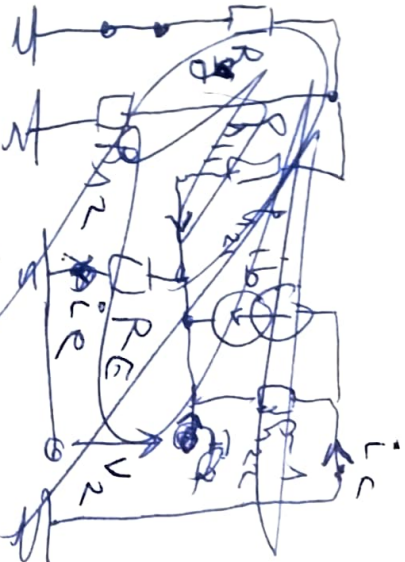

$V_2 = R_E (i_2 + i_e)$ — ①

5

$V_2 = -R_{22}^{-1} (i_c - h_{21} i_b)$ — ②

$V_2 = ((R_g \parallel R_{12}) + h_{11}) \cdot i_b$ — ③

$i_e = i_c + i_b$ — ④

③ $\Rightarrow i_b = \frac{-V_2}{(R_g \parallel R_{12}) + h_{11}}$ — ⑤

⑤ \rightarrow ② =

$V_2 = -R_{22}^{-1} i_c + h_{21} R_{22}^{-1} V_2$
 $V_2 = \frac{h_{21} R_{22}^{-1} V_2}{(R_g \parallel R_{12}) + h_{11}} + 1$

$\Rightarrow i_c = \frac{R_{22} R_{22}^{-1} V_2}{(R_g \parallel R_{12}) + h_{11}} + 1$

⑤ & ⑥ \rightarrow ④ = $\frac{R_{22} R_{22}^{-1} V_2}{(R_g \parallel R_{12}) + h_{11}} + 1$
 $i_e = \frac{1}{(R_g \parallel R_{12}) + h_{11}} + \frac{R_{22} R_{22}^{-1} V_2}{(R_g \parallel R_{12}) + h_{11}} + 1$

⑦

8

⑦ → ① =


$$V_2 = R_E i_2 \left[\frac{1}{\beta_{21} R_{21} + R_{11}} + \frac{\beta_{21} R_{21}^{-1}}{\beta_{21} R_{21} + R_{11}} - 1 \right] V_2$$

$$R_S \frac{V_2}{i_2} = \frac{R_E}{1 + R_E \left[\frac{1}{\beta_{21} R_{21} + R_{11}} + \frac{\beta_{21} R_{21}^{-1}}{\beta_{21} R_{21} + R_{11}} + 1 \right]}$$

A.N.: =

$$R_S = 7,68 \Omega$$

⑤ Gain en courant de sortie (R_L = ∞)

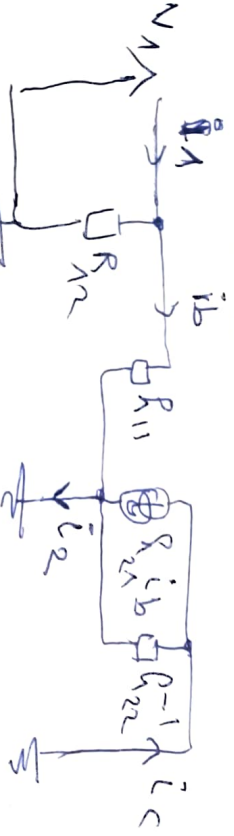

$$V_1 = R_{N2} (i_1 - i_b)$$

$$V_2 = R_{11} i_b$$

①

$$i_2 = i_b + i_c, \quad i_c = \beta_{21} i_b$$

$$\text{con: } V_{R_{21}} = 0$$

$$\Rightarrow i_2 = i_b + \beta_{21} i_b \quad \text{--- (3)}$$

$$\Rightarrow i_2 = (\beta_{21} + 1) i_b \quad \text{--- (3)}$$

$$\Rightarrow R_{N2} i_1 = (\beta_{21} + 1) i_b \quad \text{--- (4)}$$

$$\frac{(3)}{(4)} = G_{is} = \frac{i_2}{i_1} = \frac{(\beta_{21} + 1) R_{N2}}{R_{N2} + R_{11}}$$

$$\text{A.N.: } G_{is} = 150$$

⑥ schéma équivalent:



$$G_{is} = \frac{i_L}{i_1}$$

$$i_L = \frac{R_S}{R_S + R_L} \cdot G_{is} i_1$$

$$\text{A.N.: } G_{is} = 2,4 \Rightarrow G_{is} = G_{is} \cdot \frac{R_S}{R_S + R_L}$$

7

8