 


## Assignment N° 3

### Encoders, Decoders, Converters, Multiplexers, Demultiplexers

**Exercise 01:**

Consider a combinational circuit with 5 input lines and 3 output lines, as shown in the figure below



It functions as follows:

- When only one input line among  $E_0, E_1, E_2, E_3$  is at high level ( $=1$ ), its number (0, 1, 2 or 3) is coded in binary on the outputs BA.
  - If several lines are simultaneously high ( $=1$ ), the circuit codes the highest input number.
  - If all the input lines are at low level ( $=0$ ), the circuit codes  $BA=00$ , but it is signaled by  $E_{OUT}=1$  that means this code is not valid. In all other cases  $E_{OUT}=0$ .
  - The operations described so far is observed when  $E_{IN}=1$ . If  $E_{IN}=0$ , we have:  $B=A=E_{OUT}=0$ .
- 1- Give the truth table of this combinational circuit (priority encoder).
  - 2- Give the logical expressions of the outputs A, B and  $E_{OUT}$  according to the inputs  $E_0, E_1, E_2, E_3$  and  $E_{IN}$ .
  - 3- Deduce the logic circuit of this encoder.
  - 4- How can get an 8-input priority encoder from two priority encoders and some necessary logic gates.

**Exercise 02:** Parity of a number


We want to design a circuit that detects the parity of a binary number represented in 3 bits  $(ABC)_2$ . The output P will be 0 if the number of  $(ABC)_2$  in input is even and 1 otherwise.

1. Write the corresponding truth table.
2. Use an 8x1 multiplexer to realize this function.

**Exercise 03:**

Consider the assembly in the figure. It is made from three multiplexers MUX-1, MUX-2 and MUX-3 each with 4 inputs.

- 1- Give the general scheme of MUX 4 to 1 and its truth table.
- 2- Give the logical expression of Z as a function of A, B, C, D and E.
- 3-Write this expression only with exclusive OR (XOR).

 

**Exercise 04:**

A. Perform the following Boolean functions using a decoder (3 to 8) and logic gates:

$$F1 = \bar{A}\bar{B}\bar{C} \quad F2 = A\bar{B}\bar{C} \quad F3 = ABC\bar{C} + \bar{B}\bar{C}D$$

B. Using an 8 to 1 multiplexer and logic gates, perform the following logic function

$$F4 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D$$

C. Perform the following Boolean function using a decoder (3 to 8) and logic gates:

$$F5 = AB + A\bar{B}C + ABC$$

D. Using a 4 to 1 multiplexer and logic gates, perform the following logic function

$$F6 = \bar{A}\bar{B}\bar{C}D + \bar{A}BC + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D$$

E. Using a 1 to 8 demultiplexer and logic gates, perform the following logic function

$$F4 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D$$

F. Implement a multiplexer (MUX 4 to 1) using two multiplexer (MUX 2 to 1)

**Exercise 05:**

1- The Figure-1 shows a comparator of two 1-bit binary numbers  $x_i$  and  $y_i$ .

- Give the logical expressions of the outputs  $S_i$ ,  $I_i$ ,  $E_i$ ?

2- We want to design a comparator of two three-bit binary numbers  $X=x_2x_1x_0$  and  $Y=y_2y_1y_0$ , whose block diagram is given in the figure-2. Note that  $x_0$  and  $y_0$  are the least significant bits.

- Give the logical expressions of the outputs S, I and E according to the outputs  $S_i$ ,  $I_i$ ,  $E_i$  of the 1-bit comparator, with  $i=0, 1, 2$ .

3- We want to display the outputs (S, I, E) of the comparator on a 7-segment display with common cathodes using a converter, as shown in the figure-3a, and this to obtain the display given by the figure-3b.

- Give the transcoding table and logical expressions allowing the passage from the S, I, E code to the 7-segment code.

 


Figure-1

 


Figure-2

 


Figure-3a

 


Figure-3b

**Exercise 06 :** Consider a decoder with 2 selection (address) inputs ( $a_1a_0$ ) and a validation input E.

- 1- Give: the truth table and the detailed equations of its outputs  $S_0$ ,  $S_1$ ,  $S_2$ , and  $S_3$ .
- 2- Give the detailed diagram of this decoder.
- 3- Design a 4 to 16 decoder using 3 to 8 decoders?

**Exercise 07 :**

- Design a circuit that converts BCD code to 3-excess binary code.
- Give the truth table and the logic circuit of a converter of 3-bit natural binary code to Gray code.
- Using 4-bits comparators 7485 design a 32-bits comparator