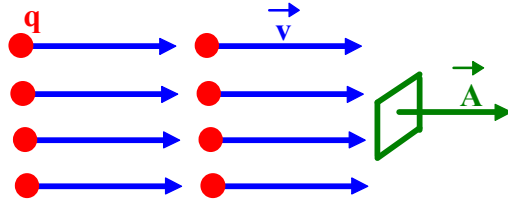


Charge Transport and Current Density

Consider n particles per unit volume all moving with velocity \mathbf{v} and each carrying a charge q .



The number of particles, ΔN , passing through the (**directed**) area \mathbf{A} in a time Δt is $\Delta N = n\vec{v} \cdot \vec{A}\Delta t$ and the amount of charge, ΔQ , passing through the (**directed**) area \mathbf{A} in a time Δt is

$$\Delta Q = nq\vec{v} \cdot \vec{A}\Delta t.$$

The **current**, $\mathbf{I}(\mathbf{A})$, is the amount of charge per unit time passing through the (**directed**) area \mathbf{A} :

$$I(\vec{A}) = \frac{\Delta Q}{\Delta t} = nq\vec{v} \cdot \vec{A} = \vec{J} \cdot \vec{A},$$

where the "**current density**" is given by $\vec{J} = nq\vec{v}_{drift}$.

The current \mathbf{I} is measured in **Ampere's** where 1 Amp is equal to one Coulomb per second (**1A = 1C/s**).

For an infinitesimal area (**directed**) area $d\mathbf{A}$:

$$dI = \vec{J} \cdot d\vec{A} \quad \text{and} \quad \vec{J} \cdot \hat{n} = \frac{dI}{dA}.$$

The "**current density**" is the amount of current per unit area and has units of **A/m²**. The current passing through the surface S is given by

$$I = \int_S \vec{J} \cdot d\vec{A}.$$

The current, \mathbf{I} , is the "flux" associated with the vector \mathbf{J} .

Electrical Conductivity and Ohms Law

Free Charged Particle:




For a free charged particle in an electric field,

$$\vec{F} = m\vec{a} = q\vec{E} \quad \text{and thus} \quad \vec{a} = \frac{q}{m}\vec{E}.$$

The **acceleration is proportional to the electric field strength E** and the **velocity of the particle increases with time!**

Charged Particle in a Conductor:

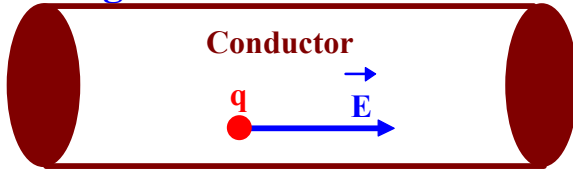

However, for a charged particle in a conductor the **average velocity is proportional to the electric field strength E** and since $\vec{J} = nq\vec{v}_{ave}$

we have


$$\vec{J} = \sigma \vec{E},$$

where σ is the **conductivity** of the material and is a property of the conductor. **The resistivity $\rho = 1/\sigma$.**

Ohm's Law:

$$\vec{J} = \sigma \vec{E}$$

$$I = JA = \sigma EA$$

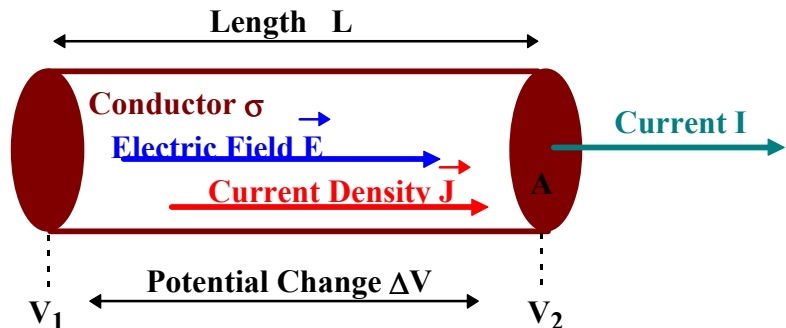

$$\Delta V = EL = \frac{I}{\sigma A} L = \left(\frac{L}{\sigma A} \right) I = RI$$

$\Delta V = IR$ (Ohm's Law) $R = L/(\sigma A) = \rho L/A$ (Resistance)
Units for R are Ohms $1\Omega = 1V/1A$

Resistors in Series & Parallel

Parallel:

In this case $\Delta V_1 = \Delta V_2 = \Delta V$

and $I = I_1 + I_2$. Hence,

$$I = I_1 + I_2 = \Delta V_1/R_1 +$$

$$\Delta V_2/R_2 = (1/R_1 + 1/R_2)\Delta V$$


so $1/R = I/\Delta V = 1/R_1 + 1/R_2$,

where I used $I_1 = \Delta V_1/R_1$ and

$I_2 = \Delta V_2/R_2$. Also,

$$\Delta V = I_1 R_1 = I_2 R_2 = IR \text{ so}$$
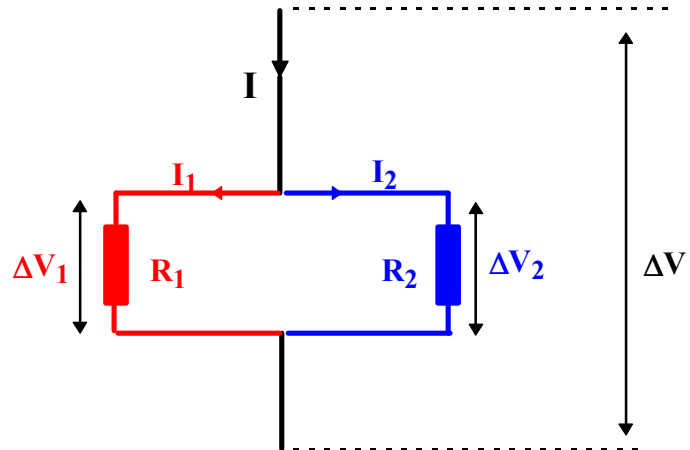
$$I_1 = R_2 I / (R_1 + R_2) \text{ and } I_2 = R_1 I / (R_1 + R_2).$$



Resistors in parallel add inverses.

Series:


In this case $\Delta V = \Delta V_1 + \Delta V_2$ and $I = I_1 = I_2$.

Hence,

$$\Delta V = \Delta V_1 + \Delta V_2 = I_1 R_1 + I_2 R_2 = (R_1 + R_2)I$$


so $R = \Delta V/I = R_1 + R_2$, where I used

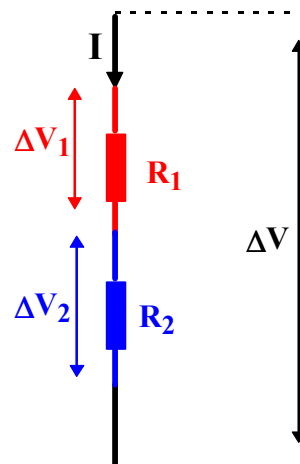$\Delta V_1 = I_1 R_1$ and $\Delta V_2 = I_2 R_2$.



Resistors in series add.

Direct Current (DC) Circuits

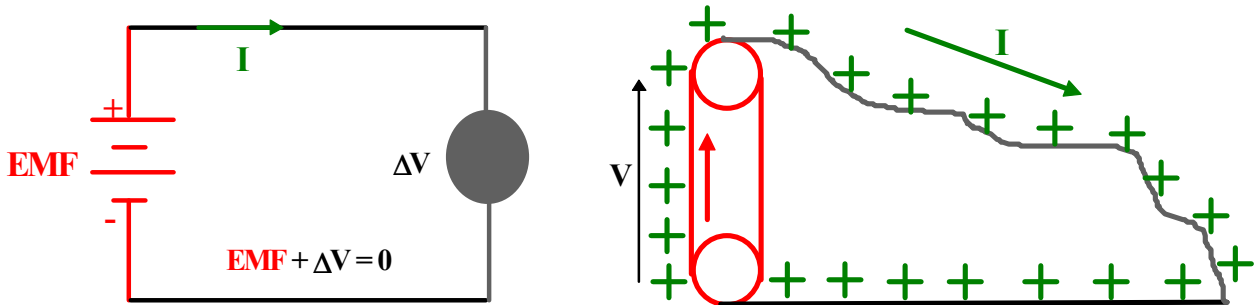

Electromotive Force:


The **electromotive force EMF** of a source of electric potential energy is defined as the amount of **electric energy per Coulomb of positive charge** as the charge passes through the source from low potential to high potential.

$$\mathbf{EMF = \varepsilon = U/q} \quad (\text{The units for EMF is Volts})$$

Single Loop Circuits:

$$\varepsilon - IR = 0 \quad \text{and} \quad \mathbf{I = \varepsilon / R}$$

(Kirchhoff's Rule)

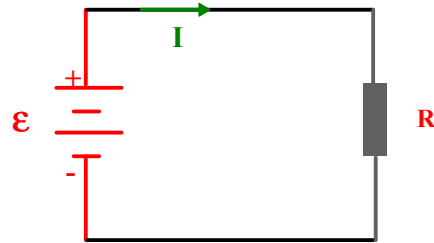


Power Delivered by EMF ($\mathbf{P = \varepsilon I}$):

$$dW = \varepsilon dq \quad P = \frac{dW}{dt} = \varepsilon \frac{dq}{dt} = \varepsilon I$$

Power Dissipated in Resistor ($\mathbf{P = I^2 R}$):

$$dU = \Delta V_R dq \quad P = \frac{dU}{dt} = \Delta V_R \frac{dq}{dt} = \Delta V_R I$$

DC Circuit Rules

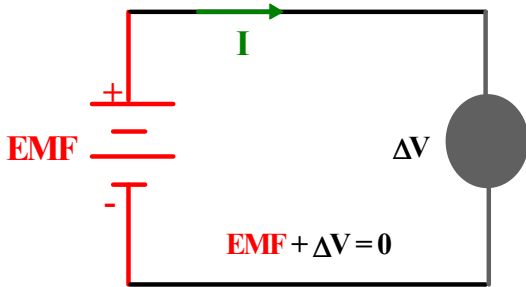

Loop Rule:


The algebraic sum of the **changes in potential** encountered in a complete traversal of any **loop** of a circuit must be **zero**.

$$\sum_{loop} \Delta V_i = 0$$

Junction Rule:



The sum of the currents entering any **junction** must be equal the sum of the currents leaving that junction.

$$\sum_{in} I_i = \sum_{out} I_i$$

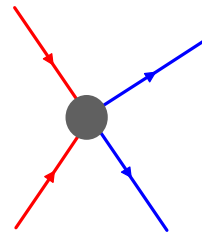

Resistor:

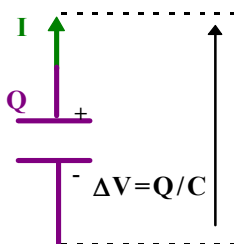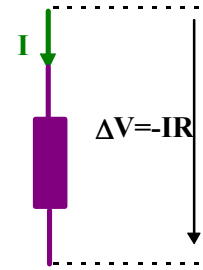If you move across a **resistor in the direction of the current flow** then the potential change is **$\Delta V_R = - IR$** .



Capacitor:

If you move across a **capacitor from minus to plus** then the potential change is


$$\Delta V_C = Q/C,$$

and the current **leaving the capacitor** is **$I = -dQ/dt$** .


Inductor (Chapter 31):

If you move across an **inductor in the direction of the current flow** then the potential change is

$$\Delta V_L = - L dI/dt.$$

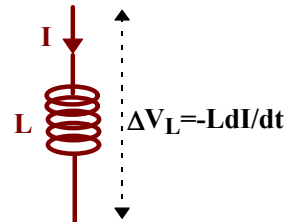

Charging a Capacitor

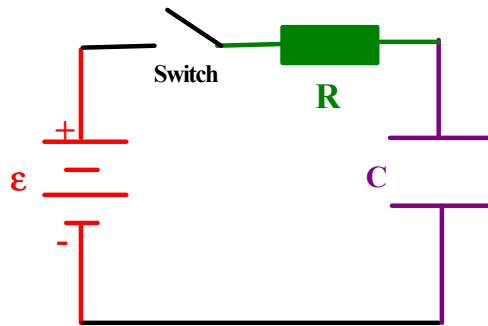

After the switch is closed the current is entering the capacitor so that $I = dQ/dt$, where Q is the charge on the capacitor and summing all the potential changes in going around the loop gives

$$\varepsilon - IR - \frac{Q}{C} = 0 ,$$

where $I(t)$ and $Q(t)$ are a function of time. If the switch is closed at $t=0$ then $Q(0)=0$ and

$$\varepsilon - R \frac{dQ}{dt} - \frac{Q}{C} = 0 ,$$

which can be written in the form


$$\frac{dQ}{dt} = -\frac{1}{\tau}(Q - \varepsilon C) , \quad \text{where I have define } \tau = RC.$$

Dividing by $(Q-\varepsilon C)$ and multiplying by dt and integrating gives

$$\int_0^Q \frac{dQ}{(Q - \varepsilon C)} = -\int_0^t \frac{1}{\tau} dt , \quad \text{which implies } \ln\left(\frac{Q - \varepsilon C}{-\varepsilon C}\right) = -\frac{t}{\tau} .$$

Solving for $Q(t)$ gives

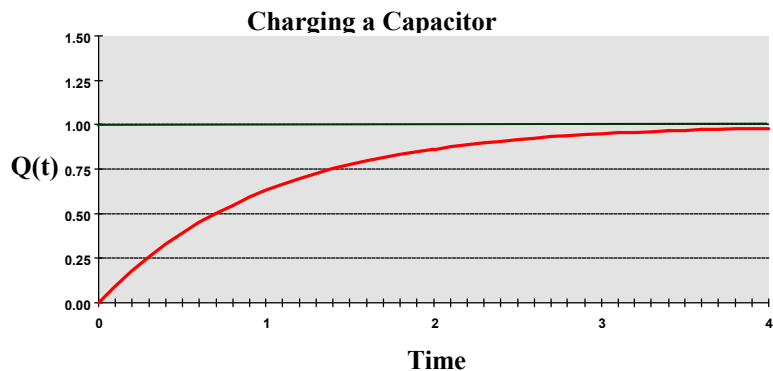
$$Q(t) = \varepsilon C(1 - e^{-t/\tau})$$



The current is given by $I(t) = dQ/dt$ which yields

$$I(t) = \frac{\varepsilon C}{\tau} e^{-t/\tau} = \frac{\varepsilon}{R} e^{-t/\tau} .$$
 The quantity $\tau = RC$ is call the **time constant** and has dimensions of time.

Discharging a Capacitor

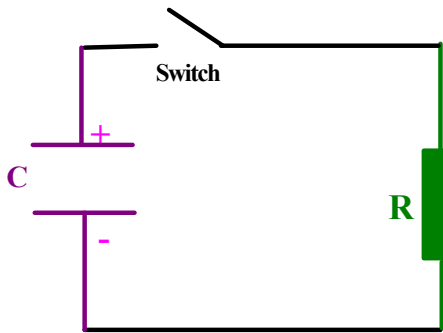

After the switch is closed the current is leaving the capacitor so that $I = -dQ/dt$, where Q is the charge on the capacitor and summing all the potential changes in going around the loop gives

$$\frac{Q}{C} - IR = 0 ,$$

where $I(t)$ and $Q(t)$ are a function of time. If the switch is closed at $t=0$ then $Q(0)=Q_0$ and

$$\frac{Q}{C} + R \frac{dQ}{dt} = 0 ,$$

which can be written in the form

$$\frac{dQ}{dt} = -\frac{1}{\tau} Q , \quad \text{where I have defined } \tau = RC .$$

Dividing by Q and multiplying by dt and integrating gives

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\int_0^t \frac{1}{\tau} dt , \quad \text{which implies } \ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{\tau} .$$


Solving for $Q(t)$ gives

$$Q(t) = Q_0 e^{-t/\tau} .$$

The current is given by $I(t) = -dQ/dt$ which yields

$$I(t) = \frac{Q_0}{RC} e^{-t/\tau} .$$

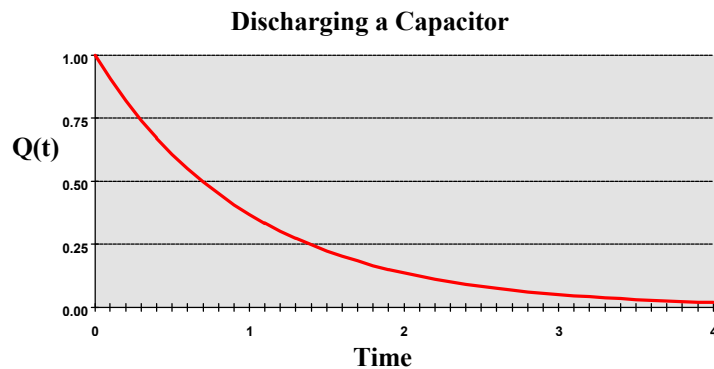The quantity $\tau = RC$ is call the "**time constant**" and has dimensions of **time**.



RL Circuits

"Building-Up" Phase:

Connecting the switch to **position A** corresponds to the **"building up" phase of an RL circuit**. Summing all the potential changes in going around the loop gives

$$\varepsilon - IR - L \frac{dI}{dt} = 0 ,$$

where **I(t)** is a function of time. If the switch is closed (**position A**) at $t=0$ and **I(0)=0** (assuming the current is zero at $t=0$) then

$$\frac{dI}{dt} = - \frac{1}{\tau} \left(I - \frac{\varepsilon}{R} \right) , \quad \text{where I have define } \tau=L/R.$$

Dividing by $(I-\varepsilon/R)$ and multiplying by dt and integrating gives

$$\int_0^I \frac{dI}{(I - \varepsilon / R)} = - \int_0^t \frac{1}{\tau} dt , \quad \text{which implies } \ln \left(\frac{I - \varepsilon / R}{-\varepsilon / R} \right) = - \frac{t}{\tau} .$$



Solving for **I(t)** gives

$$I(t) = \frac{\varepsilon}{R} (1 - e^{-t/\tau}) .$$

The potential change across the inductor is given by $\Delta V_L(t) = -LdI/dt$ which yields

$$\Delta V_L(t) = -\varepsilon e^{-t/\tau} .$$

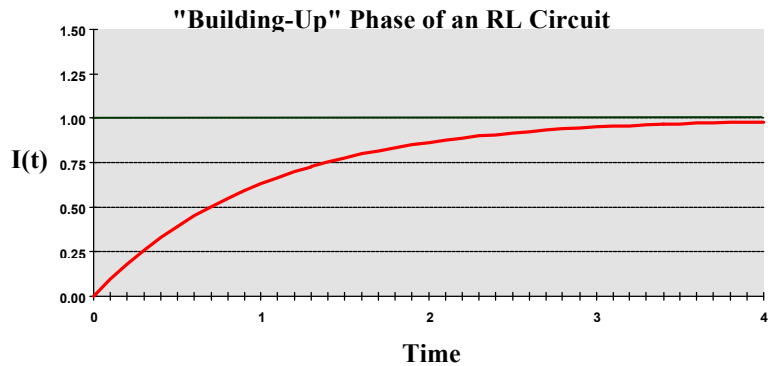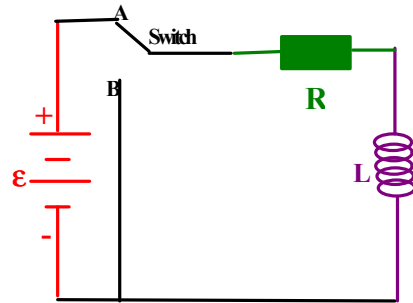The quantity $\tau=L/R$ is call the **time constant** and has dimensions of time.



"Collapsing" Phase:

Connecting the switch to **position B** corresponds to the **"collapsing" phase of an RL circuit**. Summing all the potential changes in going around the loop gives

$- IR - L \frac{dI}{dt} = 0$, where **I(t)** is a function of time. If the switch is closed (**position B**) at $t=0$ then **I(0)=I₀** and

$$\frac{dI}{dt} = - \frac{1}{\tau} I \quad \text{and} \quad I(t) = I_0 e^{-t/\tau} .$$