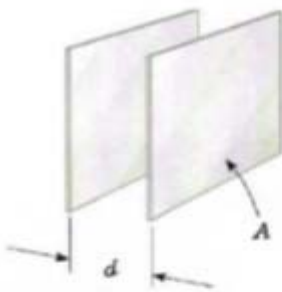


2014/2 ENGINEERING DEPARTMENTS PHYSICS 2
RECITATION 4
(CAPACITANCE AND DIELECTRICS/ CURRENT&RESISTANCE and DIRECT
CURRENT CIRCUITS)

1. An air-filled capacitor consists of two parallel plates, each with an area of **200 cm²**, separated by a distance of **0.4 cm**.
 - a) Calculate the capacitance.
 - b) If the capacitor had been connected to a 500-V battery, calculate the charge on each plate, the stored energy, the electric field between the plates and the energy density of the capacitor.
 - c) If air had been replaced with a liquid of dielectric constant $\kappa = 2.6$, how much charge would have been flowed to the capacitor from the 500-V battery?



$$A = 200 \text{ cm}^2 = 2 \cdot 10^{-2} \text{ m}^2$$

$$d = 0.4 \text{ cm} = 4 \cdot 10^{-2} \text{ m}$$

a)

$$C_0 = \epsilon_0 \frac{A}{d}$$

$$C_0 = 8.85 \cdot 10^{-12} \cdot \frac{2 \cdot 10^{-2}}{4 \cdot 10^{-2}}$$

$$C_0 = 4.4 \cdot 10^{-11} \text{ (F)}$$

$$C_0 = 44 \text{ (pF)}$$

b)

$$C_0 = \frac{Q_0}{\Delta V}$$

$$Q_0 = C_0 \Delta V$$

$$Q_0 = 4.4 \cdot 10^{-11} \cdot 500$$

$$Q_0 = 2.2 \cdot 10^{-8} \text{ (C)}$$

$$Q_0 = 22 \text{ (nC)}$$

$$U_0 = \frac{Q_0^2}{2C_0} \quad \text{or} \quad U_0 = \frac{1}{2} C_0 (\Delta V)^2$$

$$U_0 = \frac{(2.2 \cdot 10^{-8})^2}{2 \cdot 4.4 \cdot 10^{-11}}$$

$$U_0 = 5.5 \cdot 10^{-6} \text{ (J)}$$

$$U_0 = \frac{1}{2} \cdot 4.4 \cdot 10^{-11} \cdot 500^2$$

$$U_0 = 5.5 \cdot 10^{-6} \text{ (J)}$$

$$E = \frac{\Delta V}{d}$$

$$E = \frac{500}{4 \cdot 10^{-2}}$$

$$E = 1.25 \cdot 10^5 \text{ (V/m)}$$

$$E = 125 \text{ (kV/m)}$$

$$u_E = \frac{1}{2} \epsilon_0 E^2$$

$$u_E = \frac{1}{2} \cdot 8.85 \cdot 10^{-12} \cdot (1.25 \cdot 10^5)^2$$

$$u_E = 6.9 \cdot 10^{-3} \text{ (J/m}^3\text{)}$$

c)

$$C = \kappa C_0$$

$$C = 2.6 \cdot 4.4 \cdot 10^{-11}$$

$$C = 11.4 \cdot 10^{-11} \text{ (F)}$$

$$C = \frac{Q}{\Delta V}$$

$$Q = C \Delta V$$

$$Q = 11.4 \cdot 10^{-11} \cdot 500$$

$$Q = 5.7 \cdot 10^{-8} \text{ (C)}$$

$$Q = 57 \text{ (nC)}$$

$$\Delta Q = Q - Q_0$$

$$\Delta Q = 57 - 22$$

$$\Delta Q = 35 \text{ (nC)}$$

$$\Delta Q = 3.5 \cdot 10^{-8} \text{ (C)}$$

2. For the system of capacitors shown in Figure 1,

- Find the total energy stored by the group.
- When the discharge takes place on C_3 capacitor to convert to a conductor, how much charge and potential on C_1 would have been changed?


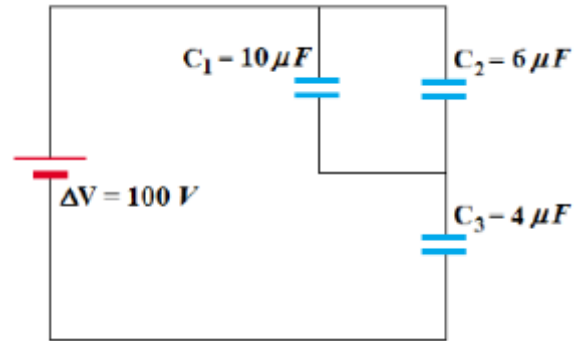


Figure 1

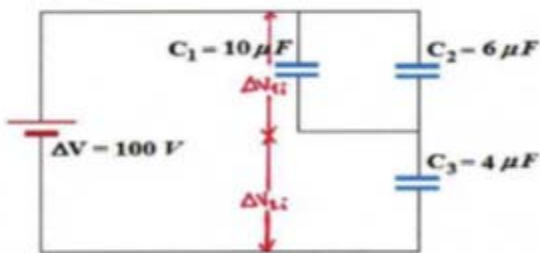

a)

$$U = \frac{1}{2} C_e (\Delta V)^2$$

$$\frac{1}{C_e} = \frac{1}{C_3} + \frac{1}{C_1 + C_2}$$

$$\frac{1}{C_e} = \frac{1}{4} + \frac{1}{10+6}$$

$$C_e = 3,2 (\mu F)$$

$$U = \frac{1}{2} 3,2 \cdot 10^{-6} \cdot 100^2$$

$$U = 1,6 \cdot 10^{-2} (J)$$

b)

$$Q = C_e \cdot \Delta V$$

$$Q = 3,2 \cdot 10^{-6} \cdot 100$$

$$Q = 3,2 \cdot 10^{-4} (C)$$

Due to the charges on capacitors connected in series are the same;

$$q_{1i} + q_{2i} = q_{3i} = Q$$

$$q_{1i} + q_{2i} = Q$$

$$C_1 \Delta V_{1i} + C_2 \Delta V_{2i} = Q$$

$$\Delta V_{1i} = \frac{Q}{C_1 + C_2}$$

$$\Delta V_{1i} = \frac{3,2 \cdot 10^{-4}}{10+6} ; \quad \Delta V_{1i} = 20 (V)$$

$$q_{1i} = C_1 \Delta V_{1i}$$

$$q_{1i} = 10 \cdot 10^{-6} \cdot 20 ; \quad q_{1i} = 2 \cdot 10^{-4} (C)$$

After turning to the conductor,

Potential difference on C_3 is equal to zero

Initial potential difference on C_1 is equal to $\Delta V_{1i} = 20 (V)$

After C_3 capacitor turns to the conductor, final potential difference on C_1 is equal to $\Delta V_f = 100 (V)$

$$\Delta V_f - \Delta V_{1i} = 100 - 20 = 80 (V)$$

$$q_{1f} = C_1 \Delta V_f$$

$$q_{1f} = 10 \cdot 10^{-6} \cdot 100 = 10 \cdot 10^{-4} (C)$$

$$\Delta q = q_{1f} - q_{1i}$$

$$\Delta q = (10 - 2) \cdot 10^{-4} ; \quad \Delta q = 8 \cdot 10^{-4} (C)$$

3. A parallel-plate capacitor has a plate separation of **1.2 cm** and a plate area of **0.12 m²**. The plates are charged to a potential difference of **120 V** and disconnected from the source. A dielectric slab having thickness **0.4 cm** and a dielectric constant of $\kappa = 2$ is inserted exactly halfway between the plates as shown in **Figure 2**.


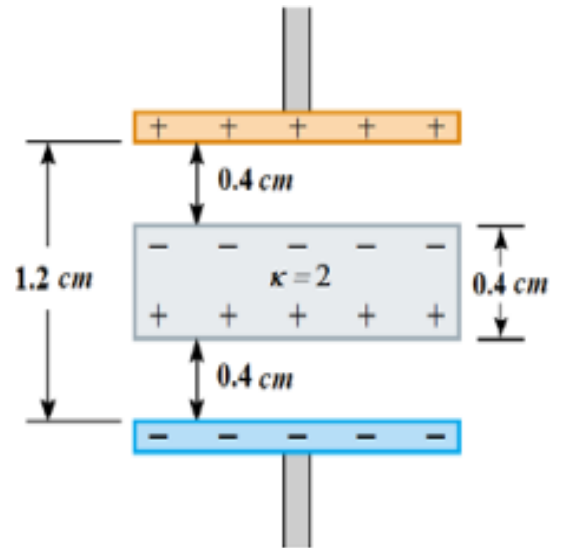


Figure 2

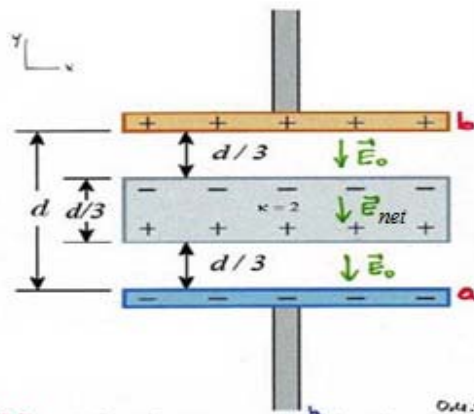

$d = 1,2 \text{ cm} = 1,2 \cdot 10^{-2} \text{ m}$
 $A = 0,12 \text{ m}^2$
 $\Delta V = 120 \text{ V}$
 $\kappa = 2$

a) $C_0 = \epsilon_0 \frac{A}{d}$
 $C_0 = 8,85 \cdot 10^{-12} \cdot \frac{0,12}{1,2 \cdot 10^{-2}}$
 $C_0 \approx 9 \cdot 10^{-11} \text{ (F)}$
 $C_0 = 90 \text{ (pF)}$

b) $\Delta V = V_b - V_a = - \int_a^b \vec{E} \cdot d\vec{s} = - \int_0^{0,4 \cdot 10^{-2}} E_0 \cdot dy \cdot \cos 180^\circ - \int_{0,4 \cdot 10^{-2}}^{0,8 \cdot 10^{-2}} E_{\text{net}} \cdot dy \cdot \cos 180^\circ - \int_{0,8 \cdot 10^{-2}}^{1,2 \cdot 10^{-2}} E_0 \cdot dy \cdot \cos 180^\circ$

$E_0 = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0}$, $E_{\text{net}} = E_0 - E_{\text{ind}} = \frac{E_0}{\kappa} = \frac{Q}{2A \epsilon_0}$

$\Delta V = \frac{Q}{\epsilon_0 A} \cdot \frac{5}{2} \int_0^{0,4 \cdot 10^{-2}} dy$

$\Delta V = \frac{5Q}{2 \epsilon_0 A} \cdot 0,4 \cdot 10^{-2} = \frac{5 \cdot Q \cdot 0,4 \cdot 10^{-2}}{2 \cdot 8,85 \cdot 10^{-12} \cdot 0,12}$

$\Delta V = 0,94 \cdot 10^{10} Q$

$C = \frac{Q}{\Delta V} = \frac{Q}{0,94 \cdot 10^{10} Q}$; $C = 1,06 \cdot 10^{-10} \text{ (F)}$
 $C = 106 \text{ (pF)}$

c) $Q = C_0 \cdot \Delta V$
 $Q = 90 \cdot 10^{-12} \cdot 120$
 $Q = 1,08 \cdot 10^{-8} \text{ (C)}$

$E_0 = \frac{Q}{A \epsilon_0}$

$E_0 = \frac{1,08 \cdot 10^{-8}}{0,12 \cdot 8,85 \cdot 10^{-12}}$

$E_0 \approx 1 \cdot 10^4 \text{ (V/m)}$

$E_{\text{net}} = \frac{Q}{2A \epsilon_0} = \frac{E_0}{\kappa}$

$E_{\text{net}} = \frac{1 \cdot 10^4}{2}$

$E_{\text{net}} = 5 \cdot 10^3 \text{ (V/m)}$

4. A conducting spherical shell has inner radius a and outer radius c . The space between these two surfaces is filled with a dielectric for which the dielectric constant is κ_1 between a and b , and κ_2 between b and c (Figure 3). Determine the capacitance of this system.

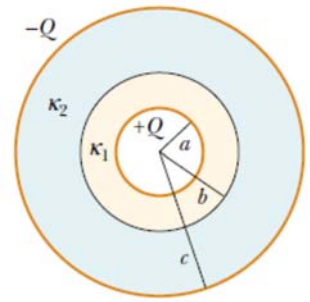


Figure 3

Electric field in the region between the conductors;

$$(c < r < a)$$

$$\oint \vec{E} \cdot d\vec{A} = \frac{q_{\text{enc}}}{\epsilon_0}$$

$$E \cdot (4\pi r^2) = \frac{Q}{\epsilon_0}$$


$$E = k \frac{Q}{r^2}$$

For the region with dielectric κ_1

$$V_b - V_a = \Delta V_{ab} = - \int_a^b \vec{E} \cdot d\vec{s}$$

$$\Delta V_{ab} = - \int_a^b k \frac{Q}{r^2} dr = -kQ \left[-\frac{1}{r} \right]_a^b = kQ \left(\frac{1}{b} - \frac{1}{a} \right)$$
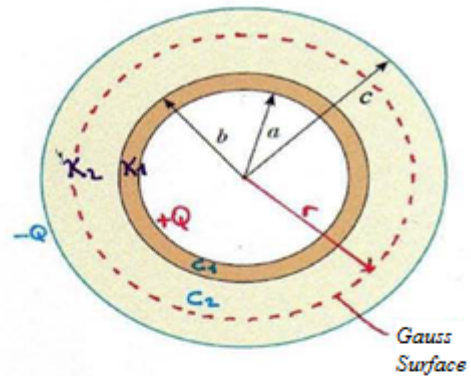
$$\Delta V_{ab} = kQ \frac{(a-b)}{ab} \quad a-b < 0 \quad \Delta V_{ab} < 0$$



For the region with dielectric κ_2

$$V_c - V_b = \Delta V_{bc} = - \int_b^c \vec{E} \cdot d\vec{s}$$

$$\Delta V_{bc} = - \int_b^c k \frac{Q}{r^2} dr = -kQ \left[-\frac{1}{r} \right]_b^c = kQ \left(\frac{1}{c} - \frac{1}{b} \right)$$

$$\Delta V_{bc} = kQ \frac{(b-c)}{bc} \quad b-c < 0 \quad \Delta V_{bc} < 0$$

$$C = \frac{Q}{|\Delta V|} ; \quad C_1 = \kappa_1 \frac{Q}{|\Delta V_{ab}|} = \kappa_1 \frac{ab}{k(b-a)}$$

$$C_2 = \kappa_2 \frac{Q}{|\Delta V_{bc}|} = \kappa_2 \frac{bc}{k(c-b)}$$

$$\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} ;$$

$$k = \frac{1}{4\pi\epsilon_0}$$

$$C_e = \frac{\kappa_1 \kappa_2 abc (4\pi\epsilon_0)}{\kappa_2 bc - \kappa_1 ab + ac(\kappa_1 - \kappa_2)}$$

5. A parallel-plate capacitor is constructed by filling the space between two square plates with blocks of three dielectric materials, as in **Figure 4**. You may assume that $\ell \gg d$

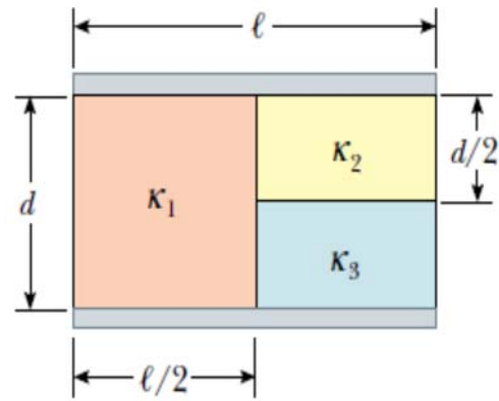


Figure 4

- a) Find an expression for the capacitance of the device in terms of the plate area A and d, κ_1, κ_2 and κ_3 .

- b) Calculate the capacitance using the values $A = 3\text{cm}^2, d = 1.5\text{mm}, \kappa_1 = 6, \kappa_2 = 3, \kappa_3 = 5$ and $\Delta V = 16\text{V}$.

- a) C_2 and C_3 capacitors are connected in series each other and parallel to C_1 capacitor

$$C_1 = \kappa_1 \epsilon_0 \frac{A/2}{d} \quad ; \quad C_2 = \kappa_2 \epsilon_0 \frac{A/2}{d/2} \quad ; \quad C_3 = \kappa_3 \epsilon_0 \frac{A/2}{d/2}$$

$$\left(\frac{1}{C_2} + \frac{1}{C_3} \right)^{-1} = \frac{C_2 C_3}{C_2 + C_3} = \frac{\epsilon_0 A}{d} \left(\frac{\kappa_2 \kappa_3}{\kappa_2 + \kappa_3} \right)$$

$$C_e = C_1 + \frac{C_2 C_3}{C_2 + C_3} = \frac{\epsilon_0 A}{d} \left(\frac{\kappa_1}{2} + \frac{\kappa_2 \kappa_3}{\kappa_2 + \kappa_3} \right)$$

- b) Using the given values;

$$C_e = \frac{8,85 \cdot 10^{-12} \cdot 3 \cdot 10^{-4}}{1,5 \cdot 10^{-3}} \left(\frac{6}{2} + \frac{3 \cdot 5}{3+5} \right) = 8,63 \cdot 10^{-12} \text{ F}$$

$$C_e = 8,63 \text{ pF}$$

$$U = \frac{1}{2} C_e (\Delta V)^2 = \frac{1}{2} 8,63 \cdot 10^{-12} \cdot (16)^2 = 1,10 \cdot 10^{-9} \text{ J}$$

$$U = 1,10 \text{ nJ}$$

6. A copper wire **2m** long and **4mm** in diameter carries a current of **6A**. If the conductor is copper with a free charge density of $8.5 \times 10^{28} (1/m^3)$ and a resistivity of $\rho = 1.6 \times 10^{-6} \Omega \text{cm}$, calculate,
- the current density,
 - the electric field,
 - the resistance,
 - the average drift velocity of free electrons,
 - the power dissipated as heat in this wire. ($e = 1.6 \times 10^{-19} \text{C}$, $\pi = 3$)

$$2r = 4 \text{ mm} = 4 \cdot 10^{-3} \text{ m}$$

$$l = 2 \text{ m}$$

$$I = 6 \text{ A}$$

$$n = 8.5 \cdot 10^{28} (1/m^3)$$

$$\rho = 1.6 \cdot 10^{-6} \Omega \cdot \text{cm} = 1.6 \cdot 10^{-8} \Omega \cdot \text{m}$$

$$A = \pi r^2 \quad (\pi = 3)$$

$$A = \pi (2 \cdot 10^{-3})^2$$

$$A = 1.26 \cdot 10^{-5} (m^2)$$

$$a) \quad J = \frac{I}{A}$$

$$J = \frac{6}{1.26 \cdot 10^{-5}}$$

$$J = 4.77 \cdot 10^5 (A/m^2)$$

$$b) \quad J = \sigma E$$

$$\sigma = \frac{1}{\rho}$$

$$J = \frac{E}{\rho}$$

$$E = \rho J$$

$$E = 1.6 \cdot 10^{-8} \cdot 4.77 \cdot 10^5$$

$$E = 7.6 \cdot 10^{-3} (V/m)$$

$$c) \quad R = \rho \frac{l}{A}$$

$$R = 1.6 \cdot 10^{-8} \frac{2}{1.26 \cdot 10^{-5}}$$

$$R = 2.54 \cdot 10^{-3} (\Omega)$$

- d) v_s : the average drift speed of free electrons in an electric field

$$J = ne v_s$$

$$v_s = \frac{J}{ne}$$

$$v_s = \frac{4.77 \cdot 10^5}{8.5 \cdot 10^{28} \cdot 1.6 \cdot 10^{-19}}$$

$$v_s = 3.51 \cdot 10^{-5} (m/s)$$

$$e) \quad P = I^2 R$$

$$P = 6^2 \cdot 2.54 \cdot 10^{-3}$$

$$P = 9.1 \cdot 10^{-2} (W)$$

1. Material with uniform resistivity ρ is formed into a wedge as shown in **Figure 5**. Find the resistance between face **A** and face **B** of this wedge.


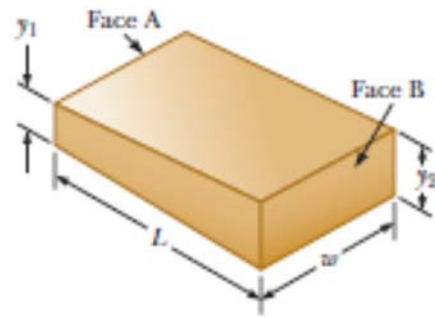


Figure 5

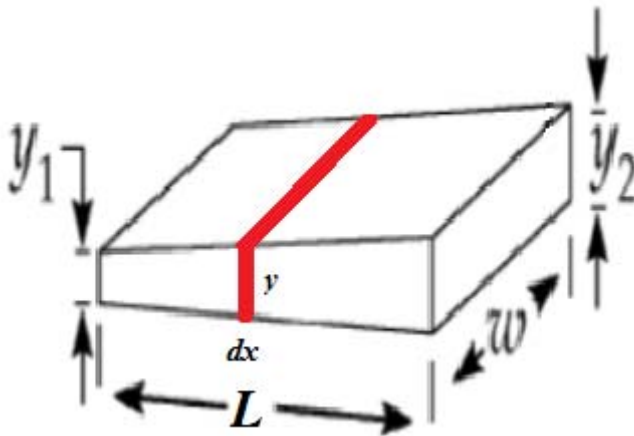

$$R = \int \frac{\rho dx}{A} = \int \frac{\rho dx}{wy}$$

where,

$$y = y_1 + \frac{y_2 - y_1}{L} x$$

$$R = \frac{\rho}{w} \int_0^L \frac{dx}{y_1 + \frac{y_2 - y_1}{L} x} = \frac{\rho L}{w(y_2 - y_1)} \ln \left[y_1 + \frac{y_2 - y_1}{L} x \right] \Bigg|_0^L$$

$$R = \frac{\rho L}{w(y_2 - y_1)} \ln \left(\frac{y_1 + y_2 - y_1}{y_1} \right)$$

$$R = \frac{\rho L}{w(y_2 - y_1)} \ln \left(\frac{y_2}{y_1} \right)$$

2. For the circuit in **Figure 6**, find
- the dissipated power for each resistance (R_1 , R_2 and R_3).
 - the power supplied by \mathcal{E}_1 and \mathcal{E}_2 generators.

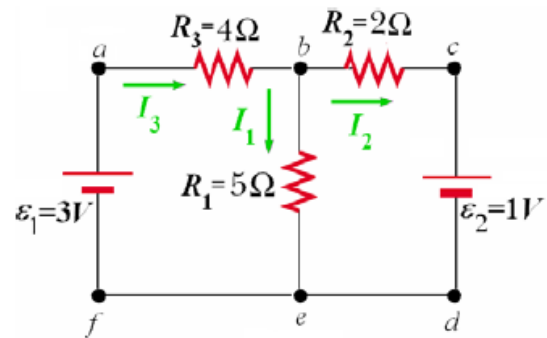


Figure 6

- Junction rule** $\sum_{\text{junction}} I = 0$
- Loop rule** $\sum_{\text{closed loop}} \Delta V = 0$

Kirchhoff's Rules

for **abefa** loop : $-I_3 R_3 - I_1 R_1 + \mathcal{E}_1 = 0$

$$-4I_3 - 5I_1 + 3 = 0 \quad (2)$$

for **bcdeb** loop : $-I_2 R_2 - \mathcal{E}_2 + I_1 R_1 = 0$

$$-2I_2 - 1 + 5I_1 = 0 \quad (3)$$

for **b** junction : $I_3 = I_1 + I_2 \quad (1)$

from (1), (2) and (3) equations; $I_1 = \frac{5}{19} \text{ (A)}$, $I_2 = \frac{3}{19} \text{ (A)}$, $I_3 = \frac{8}{19} \text{ (A)}$

$$P_{R_1} = I_1^2 R_1 = \frac{125}{361} \text{ (w)} \quad P_{R_2} = I_2^2 R_2 = \frac{18}{361} \text{ (w)} \quad P_{R_3} = I_3^2 R_3 = \frac{256}{361} \text{ (w)}$$

$$b) \quad P_{\mathcal{E}_1} = \mathcal{E}_1 I_3 = \frac{24}{19} \text{ (w)} \quad P_{\mathcal{E}_2} = \mathcal{E}_2 I_2 = \frac{3}{19} \text{ (w)}$$

3. In the circuit the capacitor is uncharged, the switch S closes at $t = 0$, as in **Figure 7**.
- a) Express the current I in the circuit as functions of time and sketch $I = f(t)$ graph.
- b) After the circuit becomes the steady-state, the switch S is opened. Find the time interval required for the charge on the capacitor to fall to one-second its initial value.

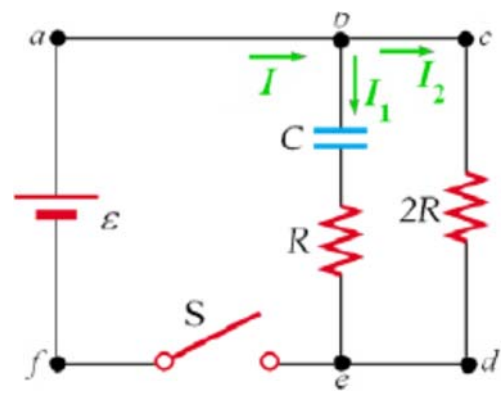


Figure 7

a) for b junction : $I = I_1 + I_2$


for acdfa loop : $\epsilon - I_2 \cdot 2R = 0$: $I_2 = \frac{\epsilon}{2R}$

$I(t) = I_1(t) + I_2$


$$I(t) = \frac{\epsilon}{R} e^{-t/RC} + \frac{\epsilon}{2R}$$

$t=0 \Rightarrow I(0) = \frac{\epsilon}{R} + \frac{\epsilon}{2R} = \frac{3}{2} \frac{\epsilon}{R}$

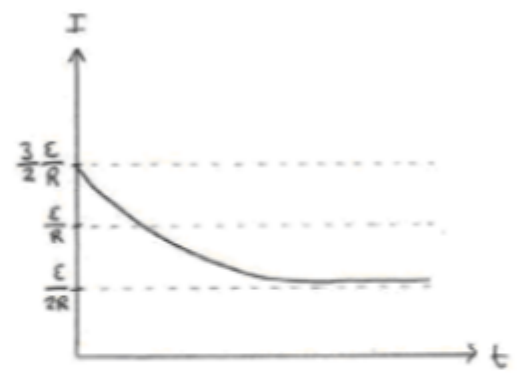$t \rightarrow \infty \Rightarrow I(\infty) = \frac{\epsilon}{2R}$ ($e^{-\infty} = 0$)



b) $q(t) = Q e^{-t/RC}$

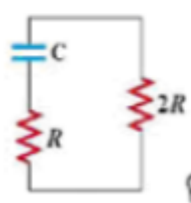

$R_e = R + 2R = 3R$

$q(t) = \frac{Q}{2}$; $\frac{Q}{2} = Q e^{-t/RC}$

$\frac{1}{2} = e^{-t/3RC}$

$\ln\left(\frac{1}{2}\right) = -\frac{t}{3RC}$

$t = -3RC \ln\left(\frac{1}{2}\right)$

$$t = 3RC \ln 2$$

4. If no charges exist on the capacitor before switch S is closed $t = 0$ as in **Figure 8**.
- Shortly after the switch S is closed, find the currents I_1 , I_2 and I_3 .
 - After the switch S has been closed for a length of time sufficiently long, find the currents I_1 , I_2 and I_3 .
 - After the switch S has been closed for long time, find the potential difference between a and b points.
 - Find the charge on the capacitor after the switch S has been closed for long time.

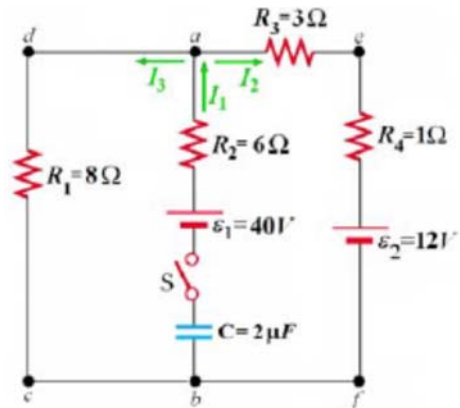


Figure 8

a) for a junction : $I_1 = I_2 + I_3$ (1)

for $adcba$ loop : $-I_3 R_1 + \varepsilon_1 - I_1 R_2 = 0$
 $-8I_3 + 40 - 6I_1 = 0$
 $6I_1 + 8I_3 = 40$ (2)

for $abfea$ loop : $I_1 R_2 - \varepsilon_1 + \varepsilon_2 + I_2 R_4 + I_2 R_3 = 0$
 $6I_1 - 40 + 12 + I_2 + 3I_2 = 0$
 $6I_1 + 4I_2 = 28$ (3)

from (1), (2) and (3) equations; $I_1 \approx 3,7(A)$ $I_2 \approx 1,5(A)$ $I_3 \approx 2,2(A)$

b) In the steady-state, there is no current through the capacitor (ab). $I_1 = 0$

for $defcd$ loop : $-I_2 R_3 - I_2 R_4 - \varepsilon_2 - I_2 R_1 = 0$
 $-3I_2 - I_2 - 12 - 8I_2 = 0$
 $I_2 = -1(A)$ $I_3 = 1(A)$

c) $V_a - I_3 R_1 = V_b$
 $V_a - V_b = 8(V)$

d) $V_a - \varepsilon_1 + V_c = V_b$ $Q = C V_c$
 $V_a - V_b = \varepsilon_1 - V_c$ $Q = 2 \cdot 10^{-6} \cdot 32$
 $8 = 40 - V_c$ $Q = 64 \cdot 10^{-6} C$
 $V_c = 32(V)$ $Q = 64 \mu C$

5. In the circuit shown in **Figure 9**,
- After the switch **S** has been closed for a length of time sufficiently long, find the currents on each resistance.
 - Find the charges for each capacitors and the dissipated power on the resistance **R₂**.
 - If the switch **S** is opened, find the time constant of the discharging circuit.
 - After the switch **S** is opened, write the current on the resistance **R₁** as a function of time.

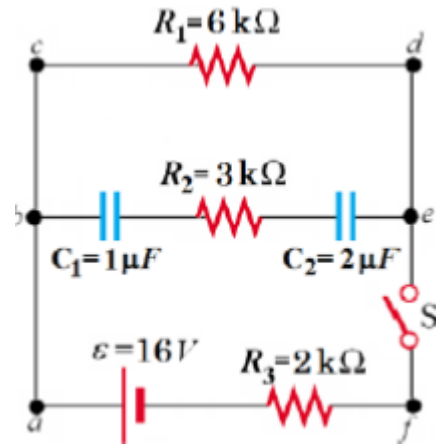


Figure 9


- a) In the steady-state, there is no current through the capacitors (be) $I_{R_2} = 0$

for **cdfac** loop : $-IR_1 - IR_3 + \mathcal{E} = 0$

$$I = \frac{\mathcal{E}}{R_1 + R_3}$$

$$I = \frac{16}{(6+2) \cdot 10^3} = 2 \cdot 10^{-3} \text{ (A)}$$

$$I_{R_1} = I_{R_3} = 2 \text{ (mA)}$$

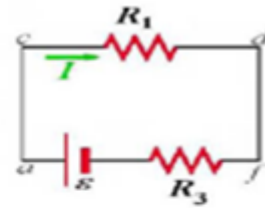

- b) for **cdebc** loop : $-IR_1 + \frac{Q}{C_1} + \frac{Q}{C_2} = 0$


$$-2 \cdot 10^{-3} \cdot 6 \cdot 10^3 + Q \left(\frac{1}{1 \cdot 10^{-6}} + \frac{1}{2 \cdot 10^{-6}} \right) = 0$$

$$Q = 8 \cdot 10^{-6} \text{ (C)}$$

$$Q = 8 \text{ (}\mu\text{C)}$$

$$P_{R_2} = I_{R_2}^2 R_2$$

$$P_{R_2} = 0 \quad (I_{R_2} = 0)$$

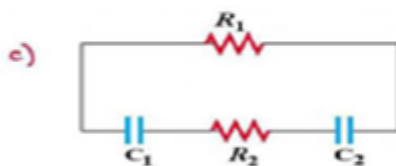

$$Z = R_e \cdot C_e$$

$$Z = 9 \cdot 10^3 \cdot 6,66 \cdot 10^{-7}$$

$$Z = 6 \cdot 10^{-3} \text{ (s)}$$

$$Z = 6 \text{ (ms)}$$

$$R_e = R_1 + R_2$$

$$R_e = 9 \text{ (k}\Omega\text{)}$$

$$\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_e = 6,66 \cdot 10^{-7} \text{ (F)}$$

d) $I(t) = -\frac{Q}{Z} e^{-t/\tau}$

$$I(t) = -\frac{8 \cdot 10^{-6}}{6 \cdot 10^{-3}} e^{-t/6 \cdot 10^{-3}}$$

$$I(t) = -\frac{4}{3} e^{-10^3 t / 6} \text{ (mA)}$$

The (-) sign in this equation means, the current is the opposite direction compared to the current **I** in the charging.