

Practical Work N°1: Electrical measurements

I- Objective of the experiment:

- How to use simple, non-digital electrical measuring devices.
- Set the measurement accuracy.
- Experimental verification of Ohm's law.

II- Theoretical principle:

We know that the reading on both the ammeter and voltmeter is related to both the caliber and ladder chosen.

$$\frac{\text{The ladder (N)}}{\text{the ladder}} \text{ reading} \longleftrightarrow \text{Caliber} \qquad X_{mes} =$$


$$\text{Reading} \longleftrightarrow X_{mes}$$

N: The number of steps of the ladder

- Ohm's law between two ends of a resistance:

It is given by the potential difference between the two ends of a conductor AB by the following relationship V

$$V_{AB} = R \times I$$

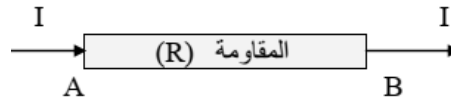

Where: V_{AB} represents the voltage.

R: is the resistance of the ohmic conductor, and its unit is ohms (Ω).

I: the intensity of the electric current, and its unit is ampere (A).

- Measurement errors

1- Direct measurements:

When we use the voltmeter and ammeter, there is uncertainty in the measurement and this is due to several sources.

Error caused by the device ΔX_{cl}

It relates to the device only, according to its design, and this is known by knowing the device type:

Device type for the voltmeter:

- 1.5 voltmeters in alternating current AC.
- 1 voltmeter in DC (direct current).

Device type for the amperimeter:

2.5 In both cases AC and DC.

$$\Delta X_{cl} = \text{device type} \times (\text{caliber} / 100)$$

The error resulting from the method ΔX_i :

Regarding both scale and caliber. We consider that the error in reading is one-quarter of the scale.

The ladder (N) ←————→ Caliber
 0.25 grade ←————→ X_l

$$\Delta X_l = 0.25 \times (\text{caliber} / \text{The ladder})$$

The total error resulting from using the device is the sum of the previous two errors

$$\Delta X = \Delta X_{cl} + \Delta X_l$$

2. Indirect errors measurements: These errors generally result from the use of mathematical relations and relations. The generality in which we find uncertainty is as follows

Let us have a function $f(x,y,z,\dots)$ multivariable, their differential is given by the following relationship:

$$df(x, y, z, \dots) = \frac{\delta f(x, y, z, \dots)}{\delta x} dx + \frac{\delta f(x, y, z, \dots)}{\delta y} dy + \frac{\delta f(x, y, z, \dots)}{\delta z} dz + \dots$$

If the function $f(x,y,z,\dots)$ A physical quantity, the uncertainty in which is given by the following relationship:

$$\Delta f(x, y, z, \dots) = \left| \frac{\delta f(x, y, z, \dots)}{\delta x} \right| \Delta x + \left| \frac{\delta f(x, y, z, \dots)}{\delta y} \right| \Delta y + \left| \frac{\delta f(x, y, z, \dots)}{\delta z} \right| \Delta z + \dots$$

Some examples

Case of addition and subtraction

If $f(x, y) = x \pm y$ then $\Delta f(x, y) = \Delta x + \Delta y$

The case of multiplication or division

If $f(x, y) = \frac{x}{y}$ Or $f(x, y) = x \cdot y$ Then $\frac{\Delta f(x, y)}{f(x, y)} = \frac{\Delta x}{x} + \frac{\Delta y}{y}$

Exercise:

Let us consider the electrical circuit shown in the following figure.


Voltmeter type: $\epsilon_{cl} = 1\%$, Caliber=10v, the ladder = 100 scales

Ampermeter type: $\epsilon_{cl} = 2.5\%$, Caliber=10mA, the ladder = 100 scales

Measured Voltage: $V_{mes} = 3.8V$

Measured intensity: $I_{mes} = 6.4 mA$

1- What is the reading on both devices?

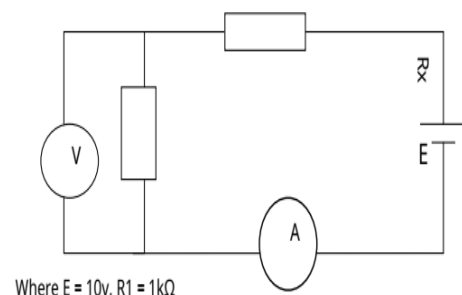

- 2- Calculate both the absolute and relative uncertainty in electrical voltage and electrical intensity?
- 3- Calculate R_X ?
- 4- Calculate ΔR_X And $\Delta R_X/R_X$?

III.Experiment:

Let the experimental structures shown in Figures 1 and 2.

- Two resistors: one variable R_X of unknown value and the other constant $R_1 = 1K \Omega \pm 1\Omega$

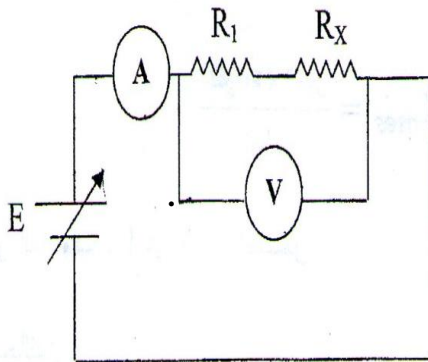


Figure.1

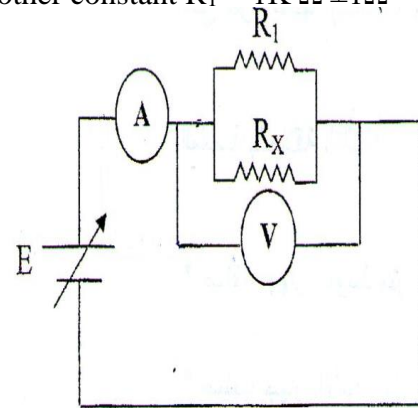


Figure.2.


Questions:

Change the potential difference from 0 to 14v, then write down the results in the table.

1. Give the method of filling the table?
2. Plot the graph $V_{mes}=f(I_{mes})$ with error barriers graphed?
3. Calculate the slope of the curve and deduce the value of R_X (exp) and compare it with the theoretical value of R_X (th)?
4. Calculate the relative uncertainty and absolute uncertainty of R_X ?
5. Write the R_X resistance in the form $R_X=(\dots\pm\dots)$?
6. Answer the same questions when performing Experiment 2?
7. Compare R_X (th) and R_X (exp) in both cases (sequence and branching)? .
8. What is your general conclusion?

ΔR_{eq}	$\Delta R_{eq} / R_{eq}$	R_{eq}	$\Delta V/V$	ΔV	V_{mes}	القراءة	السلم	العيار		$\Delta I/I$	ΔI	I_{mes}	القراءة	السلم	العيار	
									V_1							I_1
									V_2							I_2
									V_3							I_3
									V_4							I_4
									V_5							I_5

Appendix: How to read colored resistors

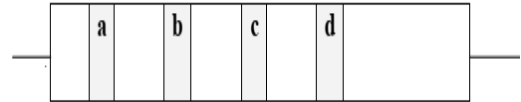

Let the colored resistor be as in the figure above. Its value can be read from the existing colors and for each color there is a number corresponding to it. Where

$$R = ab \cdot 10^c \pm d\%$$

You write the number ab . It is not a product, but rather a number. Its ones are the number b and its tens is the number a . $d\%$ represents accuracy in the design.

The number c is called the multiplier.

As for accuracy $d\%$

Silver = 10%, Gold = 5%,

Note: If the number of colors on the resistor is 6, the reading is as follows

- The first three colors: record numbers (ones, tens, hundreds)
- Fourth color: multiplier (power of ten)
- Fifth color: precision in design
- Sixth color: temperature coefficient


الرقم	اللون
2-	الفضي
1-	الذهبي
0	الأسود
1	البنّي
2	الأحمر
3	البرتقالي
4	الأصفر
5	الأخضر
6	الأزرق
7	البنفسجي
8	الرمادي
9	الأبيض

III Used equipment

- Ampermeter: with different calibers and scales (ladder), connected in series with the electrical element to be measured.
- Voltmeter: connected in parallel with the electrical element to be measured, the potential difference between its two ends
- Electric current generator: the cycle of generating alternating electric current between the two poles \sim and continuous between the two poles (+, 0, -).
- Fixed and variable resistors, connecting wires.

IV Experiment

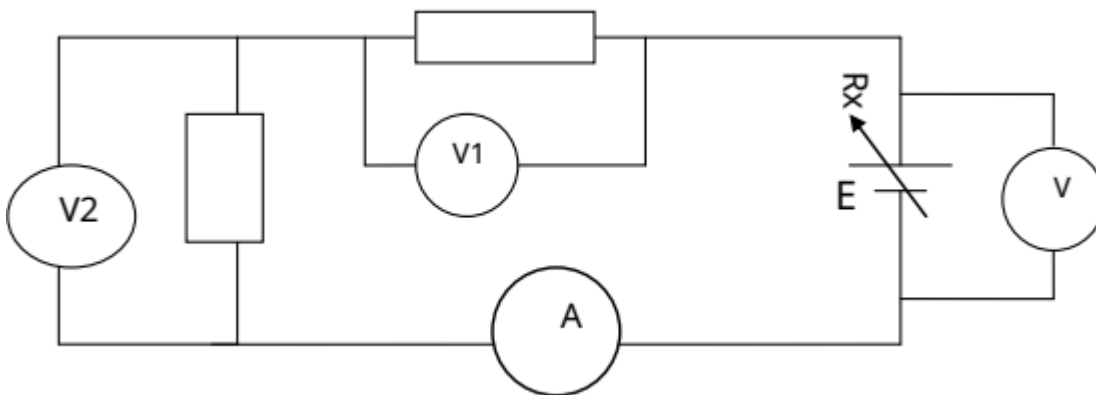
I- Achieve the electrical circuit shown in the following figure $R_1=0.1K\Omega$



Change the generator voltage E from 0 to 25V and fill out the following table

E (V)	Ampere meter			Voltmeter1			Voltmeter 2				
	Caliber	Ladder	to reading	(mA)	Caliber	The ladder reading	V1(V)	Caliber	Ladder	to reading	2(V)V
0											
5											
10											
15											
20											
25											

- 1- Notice the sum of the two voltages recorded on the two voltmeters?
 - 2- Draw the graph $V_1=f_1(I)$? Compare the value of the slope of the line with the value of R_1 ,
What do you conclude?
 - 3- Draw the graph $V_2=f_2(I)$? Calculate from the statement R_x ?
 - 4- Calculate ΔR_x And $\Delta R_x/R_x$
 - 5- Repeat the experiment using alternating current
 - 6- What is your conclusion from this experience?
- II- Achieve the electrical circuit shown in the following figure $R_2=1K\Omega$

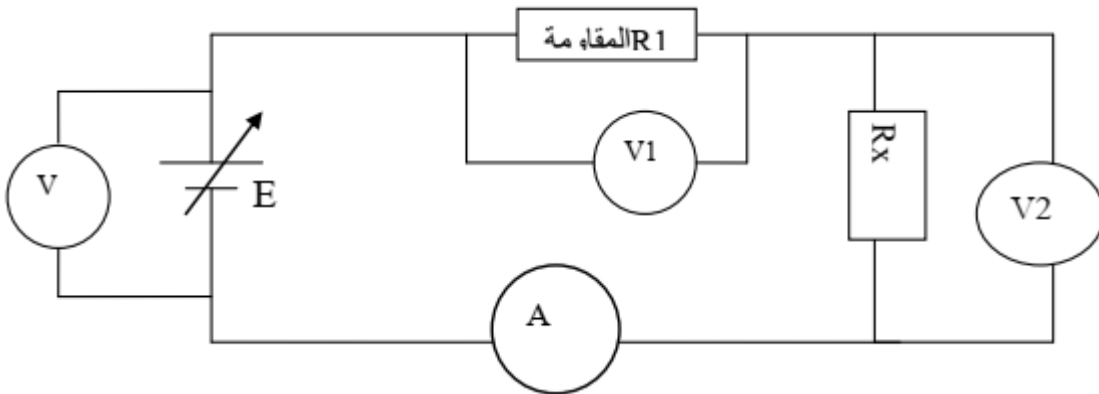

Questions:

- 1- Fill out the following table:

R1(KΩ)	V1(v)						V2(v)					
	Caliber	Alice did not	reading	V1	Δv	Δv/v	Caliber	to	reading	V2	Δv	Δv/v
0												
1												
2												
3												
4												
5												
6												
7												
8												
9												
10												

- 2- Notice the sum of the two voltages recorded on the two voltmeters?
- 3- Draw the following two graphic curves $V_1=f_1(R_1)$ and $V_2=f_2(R_1)$ on the same millimeter paper?
- 4- Interpret the curve (is it consistent with theory)?
- 5- What is your general conclusion?

